

Chapter 3 Special Section

Karnaugh Maps

Modified by M. L. Malone, Feb 05.

Note to Students

This is *hard to learn on your own*, but the many examples that we'll do in class will clarify it for you... Be patient!

2

3A.1 Introduction

- Why simplify Boolean functions?
 - Get simpler (and usually faster) digital circuits.
- How to simplify Boolean functions?
 - Use identities (laws)
 - time-consuming
 - error-prone.
 - Use Karnaugh maps (aka K-maps)

3

3A.1 Introduction

- Maurice Karnaugh
 - In 1953, a telecommunications engineer at Bell Labs.
 - Exploring the “new” field of digital logic and its application to the design of telephone circuits
 - Invented a graphical way of visualizing & then simplifying Boolean expressions.
- Karnaugh map, or K-map, named in his honor.

4

3A.2 What is a K-map?


- A matrix consisting of rows and columns that represent the output values of a Boolean function.
- Output values in each cell are derived from the *minterms* of a Boolean function.
- *minterm*
 - A **product** term that contains all of the function's variables exactly once, either complemented or not complemented.

5

3A.2 Description of K-maps and Terminology

- The minterms for a function having the inputs x and y are $\bar{x}\bar{y}$, $\bar{x}y$, $x\bar{y}$, and xy
- The minterms of the Boolean function

$$F(x, y) = xy + \bar{x}y$$

 

Minterm	x	y
$\bar{x}\bar{y}$	0	0
$\bar{x}y$	0	1
$x\bar{y}$	1	0
xy	1	1

6

3A.2 Description of K-maps and Terminology

- Minterms for a function having three inputs

Minterm	X	Y	Z
$\bar{X}\bar{Y}\bar{Z}$	0	0	0
$\bar{X}\bar{Y}Z$	0	0	1
$\bar{X}YZ$	0	1	0
$\bar{X}YZ$	0	1	1
$X\bar{Y}\bar{Z}$	1	0	0
$X\bar{Y}Z$	1	0	1
$XY\bar{Z}$	1	1	0
XYZ	1	1	1

7

3A.2 Description of K-maps and Terminology

- K-map has a cell for each minterm.
- Thus, it has a cell for each line for the truth table of a function.
- The truth table for the function $F(x,y) = xy$ is shown at the right along with its corresponding K-map.

$F(x, y) = xy$		
x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

	Y	0	1
X	0	0	0
1	0	1	

8

3A.2 Description of K-maps and Terminology

- Another example:
 - Truth table and K-map for the function, $F(x,y) = x + y$.
 - This is equivalent to the OR of all of the minterms that have a value of 1. Thus:

$$F(x, y) = x + y = \bar{X}Y + X\bar{Y} + XY$$

$F(x, y) = x + y$		
x	y	x+y
0	0	0
0	1	1
1	0	1
1	1	1

	Y	0	1
X	0	0	1
1	1	1	

9

3A.3 K-map Simplification for Two Variables

- The mintermfunction (last slide) derived from our K-map was not in simplest terms.
- 1st step in simplifying ("reducing") the expression
 - Find adjacent 1s in the K-map that can be collected into groups with sizes 1, 2, 4, 8, ... (that is, sizes that are powers of two).
- In our example, we have two such groups.
 - Can you find them?

	Y	0	1
X	0	0	1
1	1	1	

10

3A.3 K-map Simplification for Two Variables

- The number of 1s in each group is a power of two
- OK if groups overlap.

	Y	0	1
X	0	0	1
1	1	1	

11

3A.3 K-map Simplification for 2 variables: RULES

- Groupings contain only 1s
- Diagonal groups not allowed.
- Number of 1s in a group must be a power of 2 even if it contains a single 1.
- Groups must be as large as possible.**
- Groups can overlap and wrap around the sides & corners of the K-map.

12

We've identified the groupings.
Now... for EACH GROUP...

- List the minterms vertically.
- Select only the variable(s) for which the values are all alike (all 1s or all 0s) in the set of minterms. (Hint: in a column!)
 - A column of 1s represents the variable
 - A column of 0s represents its complement.
- OR the results of the groups.

	Y	0	1
X	0	0	1
1	1	1	1

We'll do this in class today!

13

3A.4 K-map Simplification for Three Variables

- We have placed each minterm in the cell that will hold its value.
- Note: Values for the yz combination at the top of the matrix form a pattern that is not a normal binary sequence: 00, 01, 11, 10.

	yz	00	01	11	10
x	0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}y\bar{z}$	$\bar{x}yz$
1	$x\bar{y}\bar{z}$	$x\bar{y}z$	$xy\bar{z}$	xyz	

14

3A.4 K-map Simplification for Three Variables

- First row contains all minterms where x is 0.
- First column contains all minterms where y and z are both zero.

	yz	00	01	11	10
x	0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}y\bar{z}$	$\bar{x}yz$
1	$x\bar{y}\bar{z}$	$x\bar{y}z$	$xy\bar{z}$	xyz	

15

3A.4 K-map Simplification for Three Variables

- Example:

$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + xyz$$
- What is the largest group of some-power-of-2 1s?
 - That is, one 1, two 1s, four 1s, eight 1s, sixteen 1s, etc.

	yz	00	01	11	10
x	0	0	1	1	0
1	0	1	1	0	

16

3A.4 K-map Simplification for Three Variables

- This grouping tells us that changes in the variables x and y have no influence upon the value of the function !
- This means that the function,

$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + xyz$$
 reduces to $F(x, y, z) = z$.

You could verify this reduction with identities or a truth table.

	yz	00	01	11	10
x	0	0	1	1	0
1	0	1	1	0	

17

3A.4 K-map Simplification for Three Variables

- Another example!

$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xyz$$
- There are (only) two groupings of 1s.
 - Can you find them?

	yz	00	01	11	10
x	0	1	1	1	1
1	1	1	0	0	1

18

3A.4 K-map Simplification for Three Variables

- OK for a group to wrap around the sides of a K-map (see **pink**).
- What does this **pink** group tell us?
 - The values of x and y are not relevant to the term of the function that is encompassed by the group.
 - What does this tell us about this term of the function?

Minterms in **pink** group:

- 000
 - 010
 - 100
 - 110
- only variable same in all is z'

		yz			
		00	01	11	10
x	0	1	1	1	1
	1	1	0	0	1

19

3A.4 K-map Simplification for Three Variables

- **Green** group?
 - Tells us that only the value of x is significant in that group.
- We see that it is complemented in that row, so the other term of the reduced function is x' .
- Our reduced function is $F(x,y,z) = x' + z'$

Recall that we had six minterms in our original function!

		yz			
		00	01	11	10
x	0	1	1	1	1
	1	1	0	0	1

20

3A.5 K-map Simplification for Four Variables

- Model can be extended to 16 minterms that are produced by a four-input function.

		YZ			
		00	01	11	10
WX	00	$\bar{w}\bar{x}\bar{y}\bar{z}$	$\bar{w}\bar{x}\bar{y}z$	$\bar{w}\bar{x}y\bar{z}$	$\bar{w}\bar{x}yz$
	01	$\bar{w}x\bar{y}\bar{z}$	$\bar{w}x\bar{y}z$	$\bar{w}xy\bar{z}$	$\bar{w}xyz$
	11	$wx\bar{y}\bar{z}$	$wx\bar{y}z$	$wxy\bar{z}$	$wxyz$
	10	$w\bar{x}\bar{y}\bar{z}$	$w\bar{x}\bar{y}z$	$w\bar{x}y\bar{z}$	$w\bar{x}yz$

21

3A.5 K-map Simplification for Four Variables

- K-map shown below has nonzero minterms indicated

$$F(w, x, y, z) = \bar{w}\bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}yz + w\bar{x}y\bar{z} + w\bar{x}yz + wx\bar{y}\bar{z} + wx\bar{y}z$$

- Can you identify (only) three groups in this K-map?

Recall that groups can overlap.

		YZ			
		00	01	11	10
WX	00	1	1		1
	01				1
	11				
	10	1	1		1

- Hint:
 - 2 groups of 4
 - 1 group of 1

22

3A.5 K-map Simplification for Four Variables

- Our three groups consist of:
 - A **purple** group entirely within the K-map at the right.
 - A **pink** group that wraps the top and bottom.
 - A **green** group that spans the corners.
- Thus we have three terms in our final function:

		YZ			
		00	01	11	10
WX	00	1	1		1
	01				1
	11				
	10	1	1		1

23

3A.5 K-map Simplification for Four Variables

The final function based on these 3 groups!


		YZ			
		00	01	11	10
WX	00	1	1		1
	01				1
	11				
	10	1	1		1

$$F(w, x, y, z) = \bar{w}\bar{x}\bar{y} + \bar{w}\bar{x}z + w\bar{y}\bar{z}$$

24

3A.5 K-map Simplification for Four Variables

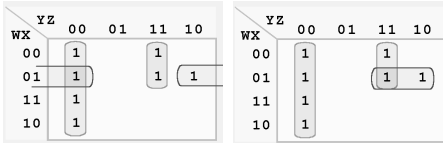- More than one solution!
- Depends on how you pick the groups of 1s.
- Keep groups as large as possible!
- See different groupings below
 - Logically equivalent!



25


More on K-Map Simplification

- What if terms are not all minterms ?
- Ex: $F(x,y,z) = x'yz + xy$
- Using Boolean laws:
 - $xy = xyz + xyz'$ because
 - $xyz + xyz' = xy(z+z') = xy(1) = xy$
- Thus, $F(x,y,z) = x'yz + xy$ is the same as
 - $F(x,y,z) = x'yz + xyz + xyz'$
- We now have all minterms in the Boolean function!

26

3A.6 Don't Care Conditions

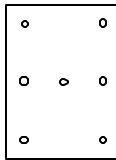- Real circuits don't always require an output for every possible input.
 - Example: Some calculator displays consist of 7-segment LEDs. These LEDs can display $2^7 - 1$ patterns, but only ten of them are useful.



27


3A.6 Don't Care Conditions

- Can design circuit so that a particular set of inputs can never happen
 - Such inputs call "don't care"s
 - Helpful in K-map circuit simplification.

28

3A.6 Don't Care Conditions

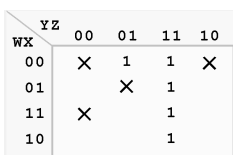- A don't care condition is identified by X in the cell of the minterm(s) for the don't care inputs
- When simplifying, we can include or ignore the Xs when creating our groups.




29

3A.6 Don't Care Conditions

- In one grouping in the K-map below, we have the function:

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

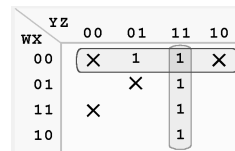

30

3A.6 Don't Care Conditions

- A different grouping gives us the function:

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11			1	
10			1	

31

3A.6 Don't Care Conditions

- The truth table of $F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$ is different from the truth table of $F(W, X, Y, Z) = \bar{W}Z + YZ$
- BUT...the values for which they differ are the inputs for which we have don't care conditions.

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11			1	
10			1	

32

3A Conclusion re K-Maps

- Provide an easy graphical method of simplifying Boolean expressions.
- Consist of the outputs of the minterms of a Boolean function.
- We discussed 2 - 3- and 4-input K-maps
 - Method can be extended to any number of inputs.

33

3A Conclusion re K-Maps

Review: Rules for K-map simplification:

- Groupings contain only 1s
- Diagonal groups not allowed.
- Number of 1s in a group must be a power of 2 even if it contains a single 1.
- Groups must be as large as possible.
- Groups can overlap and wrap around the sides & corners of the K-map.

34